

Solutions for questions 1,2 and 3

①

$$(a) v_3 = 5v_1/(15 + 5) = v_1/4, v_2 = v_1 - \mu v_3 = (4 - \mu)v_1/4$$

$$(b) v_2 = (4 - \mu)20/4 = 20 - 5\mu, i = v_2/5 + v_1/(15 + 5) = 5 - \mu$$

$$v = 4i + v_1 = 40 - 4\mu, R_{eq} = v/i = (40 - 4\mu)/(5 - \mu)$$

$$(c) \mu = 0 \Rightarrow R_{eq} = 40/5 = 8 \Omega$$

$$v_c = 0 \Rightarrow \text{short circuit so } R_{eq} = 4 + 5 \parallel (15 + 5) = 8 \Omega$$

$$(d) i = 60/(6 + R_{eq}), v = R_{eq}i = 60R_{eq}/(6 + R_{eq})$$

$$p = vi = 3600R_{eq}/(6 + R_{eq})^2$$

μ	$R_{eq}(\Omega)$	$i(A)$	$v(V)$	$p(W)$
1	9	4	36	144
5	∞	0	60	0
6	-16	-6	96	-576
7	-6	∞	$-\infty$	$-\infty$
9	-1	12	-12	-144
10	0	10	0	0

The model is invalid for $\mu = 7$, which requires infinite current from both sources.

②

$$(a) \text{ With } R_L = 0: v_{out} = 0 \text{ so } i_{in} = v_{in}/200$$

$$i_{out} = i_{in} + 49i_{in} = 50(v_{in}/200) \Rightarrow i_{out}/v_{in} = 0.25$$

$$\text{With } R_L = \infty: i_{out} = 0 \text{ so } v_{out} = 36(i_{in} + 49i_{in}) = 1800i_{in}$$

$$i_{in} = (v_{in} - v_{out})/200, v_{out} = 1800(v_{in} - v_{out})/200$$

$$v_{out} = 9v_{in} - 9v_{out} \Rightarrow v_{out}/v_{in} = 0.9$$

$$(b) i_{out-sc} = 0.25v_{in}, v_{out-oc} = 0.9v_{in}, R_t = v_{out-oc}/i_{out-sc} = 3.6 \Omega$$

$$\text{With } v_{in} = 0, v_{out} = v_t, \text{ and } i_{out} = -i_t: i_{in} = -v_t/200$$

$$i_t = v_t/36 - 49i_{in} - i_{in} = v_t/36 - 50(-v_t/200) = 10v_t/36$$

$$R_t = v_t/i_t = 36/10 = 3.6 \Omega$$

$$(c) v_{out-oc} = 0.9v_{in} = 9 \text{ V}, R_t = 3.6 \Omega,$$

$$v_{out} = R_t v_{out-oc}/(R_t + R_L) = 6.21 \text{ V}, P_{out} = v_{out}^2/R_L = 4.82 \text{ W}$$

$$i_{in} = (v_{in} - v_{out})/200 = 0.019 \text{ A}, P_{in} = v_{in}i_{in} = 0.190 \text{ W}$$

$$P_{out}/P_{in} = 4.82/0.19 = 25.4$$

③

(a)

$$(i) v(t) = \cos^2 0.125\pi t$$

$$= \frac{1}{2} [1 + \cos 0.25\pi t]$$


$$= \frac{1}{2} + \frac{1}{2} \cos 0.25\pi t$$

$$V_{avg} = \underline{\underline{\frac{1}{2} \text{ V}}} \quad V_{rms} = \sqrt{\left(\frac{1}{2}\right)^2 + \left(\frac{1/2}{\sqrt{2}}\right)^2} = \underline{\underline{0.6124 \text{ V}}}$$

$$(ii) i(t) = 12.5 \sin\left(\frac{3\pi}{4}t\right)$$

$$i_{avg} = \underline{\underline{0 \text{ A}}} \quad i_{rms} = \frac{12.5}{\sqrt{2}} = \underline{\underline{8.84 \text{ A}}}$$

③ (b)

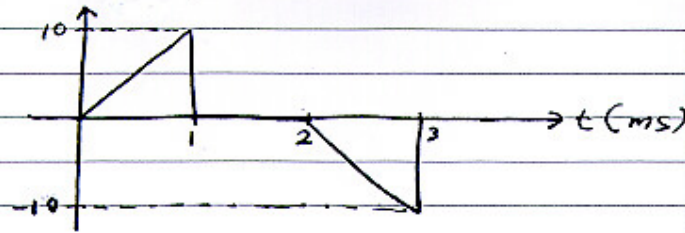Do not use
this columnAverage:

$$v(t) = \begin{cases} 10t & 0 < t < 1 \\ 0 & 1 < t < 2 \\ 20 - 10t & 2 < t < 3 \end{cases}$$

$$\begin{aligned} V_{avg} &= \frac{1}{3} \left[\int_0^1 10t \, dt + \int_2^3 (20 - 10t) \, dt \right] \\ &= \frac{1}{3} \left[5[t^2]_0^1 + 20[t]_2^3 - 5[t^2]_2^3 \right] \\ &= \frac{1}{3} [5 + 20 - 5(5)] = \underline{\underline{0 \text{ V}}} \end{aligned}$$

RMS:

$$v^2(t) = \begin{cases} 100t^2 & 0 < t < 1 \\ 0 & 1 < t < 2 \\ 400 + 100t^2 - 400t & 2 < t < 3 \end{cases}$$

$$\begin{aligned} V_{rms} &= \frac{1}{3} \left[\frac{100}{3} [1] + 400(1) + \frac{100}{3} (27 - 8) - 200(9 - 4) \right] \\ &= \frac{1}{3} \left[\frac{100}{3} + 400 + \frac{1900}{3} - 1000 \right] \\ &= 22.22 \end{aligned}$$

$$\therefore V_{rms} = \sqrt{22.22} = \underline{\underline{4.714 \text{ V}}}$$

The Solution of Question 4

When the current source is zeroed, as shown in Figure 4 (b), Z_T and I_T are calculated as:

$$\begin{aligned}
 Z_T &= 18\angle-90^\circ\Omega + \frac{(20\angle90^\circ\Omega)(31.6\angle71.6^\circ\Omega)}{51\angle78.7^\circ\Omega} \\
 &= 18\angle-90^\circ\Omega + 12.4\angle82.9^\circ\Omega = -j18\Omega + 1.53\Omega + j12.3\Omega = 1.53\Omega - j5.69\Omega \\
 &= 5.9\angle-74.9^\circ\Omega \\
 Z_T &= 5.9\angle-74.9^\circ\Omega
 \end{aligned}$$

$$I_T = V_S / Z_T = I_{C(VS)} = \frac{12\angle30^\circ\text{ V}}{5.9\angle-74.9^\circ\Omega} = 2.04\angle105^\circ\text{ A} = (-0.522 + j1.97)\text{ A}$$

$$I_T = (-0.522 + j1.97)\text{ A}$$

When the voltage source is zeroed as shown from Figure 4 (c), the impedance (Z) of L_1 , L_2 , and C branch will be computed as follows:

$$Z = j30\Omega + \frac{(20\angle90^\circ\Omega)(18\angle-90^\circ\Omega)}{j2\angle90^\circ\Omega} = j30\Omega + \frac{360\angle0^\circ\Omega}{2\angle90^\circ\Omega} = j30\Omega - j180\Omega = -j150\Omega$$

$$Z = -j150\Omega$$

$$I_{L2} = \frac{(10\angle0^\circ\Omega) * 500\angle120^\circ\text{ mA}}{(10\Omega - j150\Omega)} = \frac{(10\angle0^\circ\Omega) * 500\angle120^\circ\text{ mA}}{(150.3\angle86.2^\circ)} = 33.3\angle206^\circ\text{ mA}$$

$$I_C(I_S) = \frac{(20\angle90^\circ\Omega)}{(2\angle90^\circ\Omega)} * 33.3\angle206^\circ\text{ mA} = 333\angle206^\circ\text{ mA} = (298 - j147)\text{ mA}$$

The Total capacitor current is:

$$I_{C(\text{tot})} = I_C(V_S) = (0.821 - j1.82)\text{ A} = 2.00\angle114^\circ\text{ mA}$$

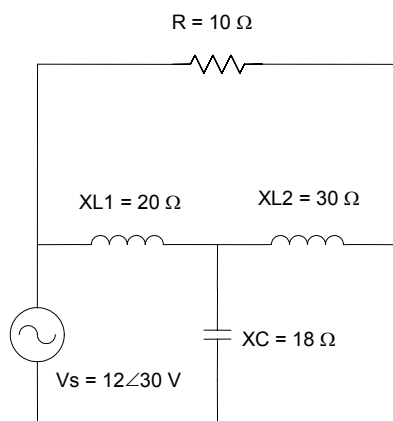


Figure 4 (b)

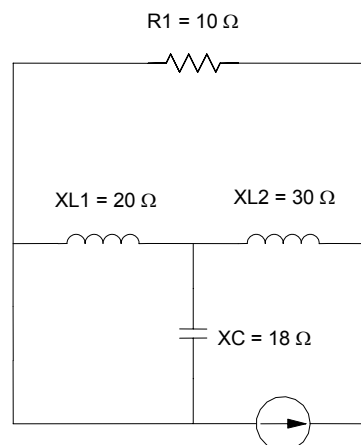


Figure 4 (c) $I_S = 0.5\angle120^\circ\text{ A}$

Solution of Question 5

The original circuit is redrawn in Figure 5 (b) for simplification combining R_1 , R_2 and X_L

$$Z_A = R_1 + R_2 \parallel X_L = 1 \angle 0^\circ \text{ k}\Omega + \frac{(3.3 \angle 0^\circ)(3 \angle 90^\circ) \text{ k}\Omega}{(3.3 \text{ k}\Omega + j3 \text{ k}\Omega)} = 2.4 \text{ k}\Omega + j1.64 \text{ k}\Omega$$

$$= 2.98 \angle 33.4^\circ \text{ k}\Omega$$

$$Z_A = 2.98 \angle 33.4^\circ \text{ k}\Omega$$

Combining R_3 and Z_A , we get:

$$Z_B = R_3 \parallel Z_A = \frac{(10 \angle 0^\circ \text{ k}\Omega)(2.98 \angle 33.4^\circ \text{ k}\Omega)}{12.62 \angle 7.5^\circ \text{ k}\Omega} = 2.37 \angle 25.9^\circ \text{ k}\Omega$$

Combining X_C and Z_B , we find:

$$Z_{TH} = X_C \parallel Z_B = \frac{(5 \angle -90^\circ \text{ k}\Omega)(2.37 \angle 25.9^\circ \text{ k}\Omega)}{4.52 \angle -62.3^\circ \text{ k}\Omega} = (2.62 \angle -1.8^\circ \text{ k}\Omega)$$

$$= 2.62 \text{ k}\Omega - j0.08 \text{ k}\Omega$$

$$Z_{TH} = (2.62 - j0.08) \text{ k}\Omega$$

$$V_{TH} = \frac{(Z_B) * V_S}{(X_C + Z_{TH})} = \frac{(2.37 \angle 25.9^\circ \text{ k}\Omega) * 50 \angle 0^\circ}{4.52 \angle -62.3^\circ \text{ k}\Omega} = 26.3 \angle 87.6^\circ \text{ V}$$

The Thevenin Circuit with R_4 connected is shown in Figure 5 (c).

$$V_{R4} = \frac{(R_4) * V_{TH}}{(R_4 + Z_{TH})} = \frac{(4.7 \angle 0^\circ \text{ k}\Omega) * 26.3 \angle 87.6^\circ \text{ V}}{7.32 \angle -0.64^\circ \text{ k}\Omega} = 16.9 \angle 88.2^\circ \text{ V}$$

$$V_{R4} = 16.9 \angle 88.2^\circ \text{ V}$$

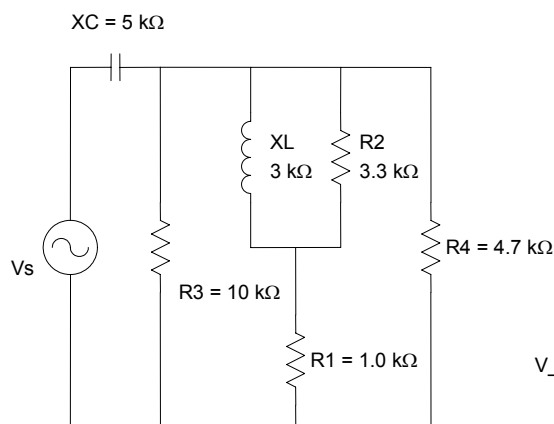


Figure 5 (b)

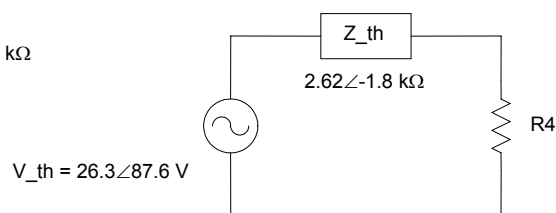


Figure 5 (c)